



# Binary Blitz

Digital Systems Laboratory Verilog GAMES Final Project



# Binary Blitz

Digital Systems Laboratory Verilog GAMES Final Project

41171213H 張慎修、41175033H 吳炳煌



## TABLE OF CONTENTS



**Motivation**

**01**

**Schedule**

**02**

**Functions/  
Design Details**

**03**

**Display**

**04**

**05**

**Obstacle**

**06**

**Future Prospects**


**07**

**Feedback**



01

# Motivation

 

# **⌞ Motivation ⌞**

**Learn Binary  
Unsigned Number**

**Enhance Logical  
Thinking**

**Improve  
Mathematical  
Skills**

**Increase  
Reaction Speed**



02

# Schedule



# ✚ MAY/JUNE CALENDAR ✚

21	22	23	24	25	26	27
28	29	30	31	1	2	3
4	5	6	7	8	9	10
11	12	13	14	15	16	17
18	19	20	21	22	23	24

## Design Thinking

Thinking the game content, function and design for someone

## Practice


Write programs ,Debug ,combine with buzzer and the concept teaching by teacher

Record/PPT  
Final presentation



03


# Functions/ Design Details

 


 
# └ Functions/Design Details ─

Connect the FPGA and buzzer using GND and PIN\_W10



Show the question on  
segment 0,1


Show the user answer  
on segment 2,3

Show the countdown  
timer second on  
segment 5

Show the pili led to increase  
the excitement

Input the switch to calculate the binary unsigned number

# ✦ Functions/Design Details ✦

 

# └ Functions/Design Details ─

```
module timer(led,clk,rst,pb,a,seg5,seg_a,seg_b,speaker,Q,out0,out1);
    input clk,rst,pb;
    input [3:0] a;
    output reg [6:0] seg5;
    output reg [7:0] seg_a, seg_b;
    output reg speaker;
    parameter clkdivider = 10000000/349/2;
    output reg [9:0] led;

    output reg [4:1] Q;
    output reg [7:0] out0;
    output reg [7:0] out1;

    reg [6:0] sec;
    reg [4:0] state, nstate;
    reg [23:0] tone;

    reg clk1,clk2;
    reg [29:0] count;//pili
    reg [22:0] counter;//timer
    reg [15:0] counter1;//buzz
```

## └ Functions/Design Details ─

```
always@(posedge clk)begin
    tone = tone + 1;
end

always @(posedge pb or negedge rst) begin
    if (!rst) begin
        Q = 4'b1000;
    end
    else begin
        Q = {Q[3:1], Q[4]^Q[3]};
        if (Q == 4'b1110) begin
            Q = 4'b1100;
        end
        else if (Q == 4'b1100) begin
            Q = 4'b1000;
        end
    end
end
end
```

# └ Functions/Design Details ─

```
//delay clock
always@(posedge clk or negedge rst or negedge pb)begin
    if(~rst)begin
        counter = 0;
        counter1 = 0;
        clk1 = 0;
    end
    else if(~pb)begin
        counter = 0;
        count = 0;
        clk1 = 0;
    end
    else if(counter==1000000)begin//timer
        counter = 0;
        clk1 = ~clk1;
    end
    else if(count==250000)begin//pili
        count = 0;
        clk2 = ~clk2;
    end
    else if(counter1 == 0)begin
        if (sec == 4'b0000)begin
            if(a != q)begin//wrong
                if(tone[22])
                    counter1 = clkdivider*1.5;
                else
                    counter1 = clkdivider;
            end
            else begin//correct
                if(tone[22])
                    counter1 = clkdivider;
                else
                    counter1 = clkdivider/3;
            end
        end
    end
    else
        counter = counter - 1;
        counter1 = counter1 - 1;
        count = count + 1;
    end
end
```

# └ Functions/Design Details ─

```
always @(posedge clk2 or negedge rst )begin
    if(~rst) state = 0;
    else state = nstate;
end

always@(posedge clk1 or negedge rst or negedge pb )begin
    if(~rst | ~pb)begin
        sec = 4'b0011;
    end

    else
        sec = sec - 1;
    end

always @(posedge clk)begin
    if(counter1 == 0)
        speaker = ~speaker;
    end

always @(state)begin
    if(state == 5'b10000)
        nstate = 5'b00001;
    else
        nstate = state + 1;
    end
end
```

# └ Functions/Design Details ─

```
always@(state)begin//pili
    case(state)
        5'b00000: led = 10'b1000000001;
        5'b00001: led = 10'b0100000010;
        5'b00010: led = 10'b0010000100;
        5'b00011: led = 10'b0001001000;
        5'b00100: led = 10'b0000110000;
        5'b00101: led = 10'b0001001000;
        5'b00110: led = 10'b0010000100;
        5'b00111: led = 10'b0100000010;
        5'b01000: led = 10'b1000000001;
        5'b01001: led = 10'b0100000010;
        5'b01010: led = 10'b0010000100;
        5'b01011: led = 10'b0001001000;
        5'b01100: led = 10'b0000110000;
        5'b01101: led = 10'b0001001000;
        5'b01110: led = 10'b0010000100;
        5'b01111: led = 10'b0100000010;
        5'b10000: led = 10'b1000000001;
        5'b10001: led = 10'b1000000001;
        5'b10010: led = 10'b1000000001;
        default: led = 10'b0000000000;
    endcase
end

always@(sec)begin//timer
    case(sec)
        4'b0000: seg5 = 7'b1000000; //0
        4'b0001: seg5 = 7'b11111001; //1
        4'b0010: seg5 = 7'b0100100; //2
        4'b0011: seg5 = 7'b0110000; //3
        default: seg5 = 7'b1111111; //all blind
    endcase
end
```



# Functions/Design Details

```
always@(a)begin//switch
  case(a)
    4'b0000: {seg_b, seg_a} = {8'b11111111, 8'b11000000}; // 0
    4'b0001: {seg_b, seg_a} = {8'b11111111, 8'b11111100}; // 1
    4'b0010: {seg_b, seg_a} = {8'b11111111, 8'b10100100}; // 2
    4'b0011: {seg_b, seg_a} = {8'b11111111, 8'b10110000}; // 3
    4'b0100: {seg_b, seg_a} = {8'b11111111, 8'b10011001}; // 4
    4'b0101: {seg_b, seg_a} = {8'b11111111, 8'b10010010}; // 5
    4'b0110: {seg_b, seg_a} = {8'b11111111, 8'b10000010}; // 6
    4'b0111: {seg_b, seg_a} = {8'b11111111, 8'b11111100}; // 7
    4'b1000: {seg_b, seg_a} = {8'b11111111, 8'b10000000}; // 8
    4'b1001: {seg_b, seg_a} = {8'b11111111, 8'b10010000}; // 9
    4'b1010: {seg_b, seg_a} = {8'b111111001, 8'b11000000}; // 10
    4'b1011: {seg_b, seg_a} = {8'b111111001, 8'b111111001}; // 11
    4'b1100: {seg_b, seg_a} = {8'b111111001, 8'b10100100}; // 12
    4'b1101: {seg_b, seg_a} = {8'b111111001, 8'b10110000}; // 13
    4'b1110: {seg_b, seg_a} = {8'b111111001, 8'b10011001}; // 14
    4'b1111: {seg_b, seg_a} = {8'b111111001, 8'b10010010}; // 15
  endcase
end
endmodule
```

```
always @(Q) begin
  case (Q)
    4'b0001: {out1, out0} = {8'b11111111, 8'b11111100}; // 01
    4'b0010: {out1, out0} = {8'b11111111, 8'b10100100}; // 02
    4'b0011: {out1, out0} = {8'b11111111, 8'b10110000}; // 03
    4'b0100: {out1, out0} = {8'b11111111, 8'b10011001}; // 04
    4'b0101: {out1, out0} = {8'b11111111, 8'b10010010}; // 05
    4'b0110: {out1, out0} = {8'b11111111, 8'b10000010}; // 06
    4'b0111: {out1, out0} = {8'b11111111, 8'b11111100}; // 07
    4'b1000: {out1, out0} = {8'b11111111, 8'b10000000}; // 08
    4'b1001: {out1, out0} = {8'b11111111, 8'b10010000}; // 09
    4'b1010: {out1, out0} = {8'b111111001, 8'b11000000}; // 10
    4'b1011: {out1, out0} = {8'b111111001, 8'b111111001}; // 11
    4'b1100: {out1, out0} = {8'b111111001, 8'b10100100}; // 12
    4'b1101: {out1, out0} = {8'b111111001, 8'b10110000}; // 13
    4'b1110: {out1, out0} = {8'b111111001, 8'b10011001}; // 14
    4'b1111: {out1, out0} = {8'b111111001, 8'b10010010}; // 15
  default: {out1, out0} = {8'b11111111, 8'b11111111};
  endcase
end
```





04

# Display





# Display



## Binary Blitz Display

Digital Systems Laboratory Verilog GFMS Final Project

41171213H 張慎修、41175033H 吳炳煌



05

Obstacle






# Obstacle


 
## Determine win/lose

When we done every part of game, we have no idea to combine them to become a game ,we got idea in that the LSFR and the input switch will make the segment change , so we deal with it



## Divide different clock

We have countdown timer ,pili led and buzzer ,we want the three part have different frequent ,we learn it has clk, clk1 in the class, so we try to add clk2 to complete the game.



06

# Future Prospects




# Future Prospects


 
## Buzzer

Add the player can adjust volume , variable tones and make rhythm and beats let the game more fun and meaning of education.



## More Player


Add more players mode with score tracking for intense binary bables, increase the game's fun and challenge.




07

# Feedback
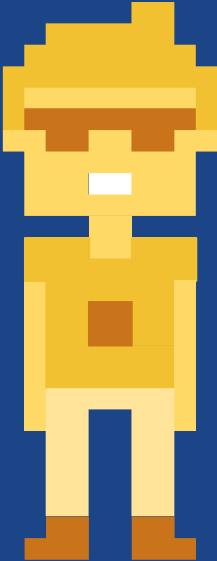
# └ FIRST ANNOUNCEMENT ─



楊同學: **It's a good idea that mini games can be fun and educating.**



吳同學: **It was very creative and also fun! I look forward to future development.**



**THANK  
YOU**

